

# I2C SENSOR TRANSMITTER (SLAVE)

## Introduction


Transmitter is a device which sends data from one point to another using different techniques and protocols. Here it is designed for interfacing analog sensors with microcontrollers. The output signal from the analog sensor is transmitted to the microcontroller in digital form using I2C protocol. The transmitter first amplifies the weak analog signal using op-amps and then implements the I2C protocol using a microcontroller to transmit the data.

### What is I2C ?

*It is an acronym for inter-integrated circuit. It is a serial multi-master multi-slave communication protocol used to communicate between peripheral ICs (slave) and the processor (master) in a short distance. It is a 2 wire communication uses 2 signal wires known as SDA (data) and SCL (clock). The slave and master devices are connected parallel to the I2C bus and each device is identified using a 7 bit address (max. 128 devices).*
 
## Project Plan

The I2C transmitter has 4 major parts; input sensor (analog), signal conditioner, analog to digital converter (ADC) and I2C interface. The input sensor is a readymade analog soil meter containing 3 sensors which are pH, moisture and light. The signal conditioner amplifies the sensor signal to a level which is required for the ADC. The ADC converts the analog signal to digital signal. The I2C interface establishes a communication with the master and sends the digital signal to the master.



## Analog Sensor

The below given image represents the chosen soil meter. It is an active sensor (no external power required) which is capable of measuring Light, Moisture and pH. It produces a small EMF for each measurement. pH and moisture measurement is done by using different electrodes. The EMF produced between the electrodes is due to the ion flow in the soil through the electrodes. There are separate electrodes for each measurement. The amount of light is measured by using a solar cell. Then, the generated EMF is given to the moving coil meter through a sensor selection switch.

### Observed Specifications

Moving coil resistance : 700Ω

Sensor output voltage range (with coil load) : 0-200 mV




Meter Reading (Moisture)	Voltage (Across moving coil meter)
1	00 mV
2	20 mV
3	40 mV
4	60 mV
5	80 mV
6	100 mV
7	120 mV
8	140 mV
9	160 mV
10	200 mV

Table 1: Signal v/s Gauge reading
 
## Signal Conditioner

The purpose of signal conditioner is to convert the sensor signal (200 mV) to a value which is required for the ADC for analog to digital conversion. It is basically an op-amp amplifier circuit. Here, the input signal is a DC signal, so a differential amplifier with a gain other than unity is used to amplify the 200 mV DC signal. It also helps to avoid the loading effect on the sensor. The given circuit is representing an ideal differential amplifier using op-amp.



### Signal conditioner design

The power supply required for the signal conditioner is 5V DC (single power supply). Here CA3140 is used for this purpose, because it works well in low voltages. It gives an output voltage swing of 3.7V at 5V input power supply. Due to this limitation, The ADC input is set at a maximum of 2.56 V. So the signal conditioner must provide a 2.5V output for the 200mV input.

$$\text{Gain, } G = \frac{2.5}{0.2} = 12.5$$

First, fix the R1 with a 560K $\Omega$  resistance.


By using the differential amplifier equation,

$$R2 = \frac{560}{12.5} = 44.8 \text{ K}\Omega$$

The value of R2 is small compared to R1, therefore a small change in the value of R2 will cause a big change in the gain. This will introduce error in the measurement. Therefore, to reduce the variation in R2 value and increase the precision by choosing 3 resistors in parallel combination.

$$R2 = 100\text{K}\Omega \parallel 100\text{K}\Omega \parallel 560\text{K}\Omega = 45.90 \approx 44.8$$

The final circuit is given below.

 

Here, inverting input (V2) is connected to the ground to eliminate the V2 term from the differential amplifier equation. So, now the V1 (input) is alone determines the output. The 680 $\Omega$  resistor in the input is used as a dummy resistor for mimicking 'moving coil meter'. Otherwise, the sensor output will change from 0-200mV range.

## Observations

The observed input and output values and the corresponding gain is given in the below table.

@  $V_{cc} = 5.55V$


Input	Output	Gain
4.0 mV	0.062 V	15.50
22.5 mV	0.294 V	13.00
40.8 mV	0.524 V	12.80
58.2 mV	0.738 V	12.65
70.7 mV	0.896 V	12.67
95.0 mV	1.195 V	12.57
115.6 mV	1.460 V	12.63
139.4 mV	1.749 V	12.55
167.3 mV	2.080 V	12.43
199.6 mV	2.480 V	12.43

## ADC and I2C Interface

It is easy to implement the ADC and I2C communication using a microcontroller. Here, the circuit need only a low sampling rate ADC (because the signal is DC), So microcontroller ADC is very good for this purpose. The whole process only require some programming to complete these processes.

ATTiny85 is a small 8 pin microcontroller containing 4 inbuilt ADC and the I2C ports.

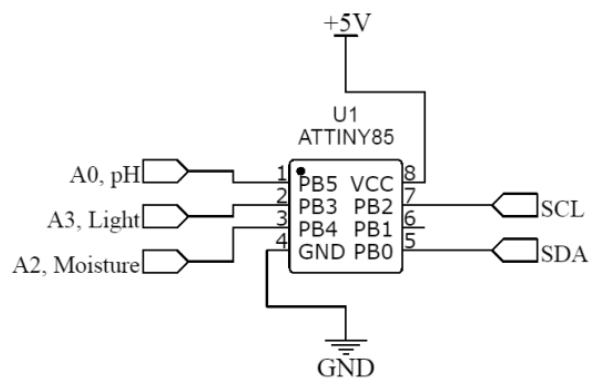
So it is selected for this project. The 3 ADC inputs are used to connect to the 3 sensors.



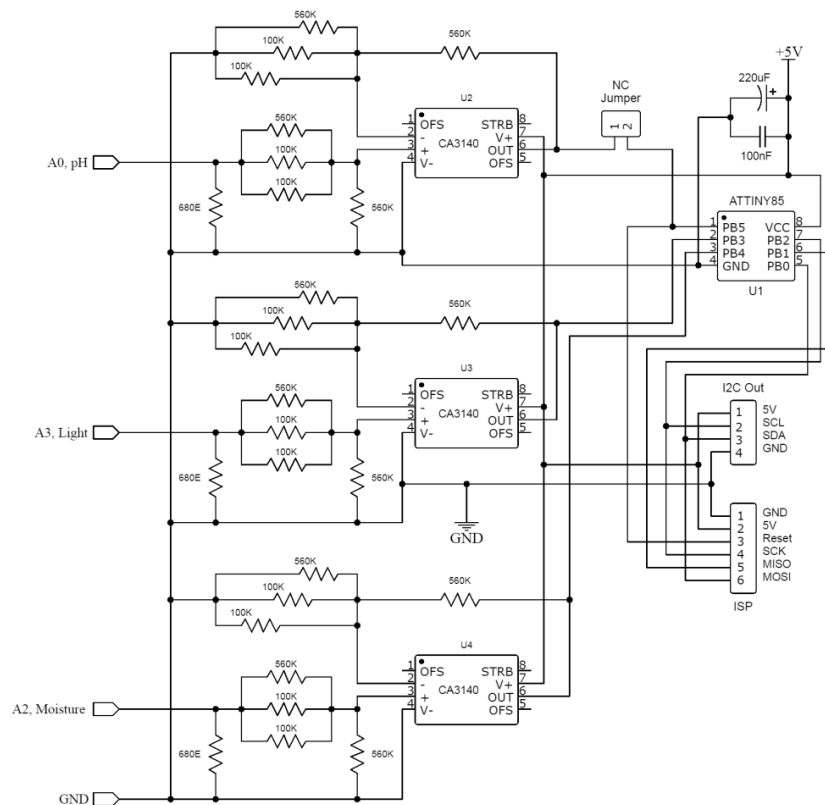
## Full Circuit Diagram

The below given circuit diagram represents the full system diagram.

Three copies of the above mentioned signal conditioner is provided for each input signal from the sensor. The negative connection from three of the sensors are connected to the GND to ensure that the input signal is in reference with the amplifier GND. The jumper in the pH sensor amplifier output is used at the event of microcontroller programming. Normally it is shorted and at the event of programming it should be in open position because, the pin 1 of the microcontroller is used for both reset and ADC functions. At normal condition it is fused as ADC, so it works as analog input (ADC) pin. But, for reprogramming the microcontroller, it is important to apply a high voltage ( $> V_{cc}$ ) in the reset pin (High voltage programming). If it is not opened at that programming time, there is a chance of damaging the op-amp and failure of the programming attempt. The I2C output port contain 4 pins. Two (SDA & SCL) for I2C communication and the other two is to provide the working voltage for the circuit. The ISP (in-system programming) is used for the programming of the microcontroller. The capacitors in the circuit is to reduce the noise in the powersupply and provide a stable voltage to the circuit.



## The Prototye

 

## Software (Language used: c++)

The below given program is the one which is uploaded in the microcontroller. It works as a slave. The slave address is fixed in this program. For connecting multiple transmitters together, it is important to change the slave address for each device. In this program, the data from the ADC is directly send to the master device. The sending is only occurred when the master requests for data. The ADC in this ATtiny85 have 10 bit resolution. So the maximum value get from the ADC is 1023 ( $2^{10}-1$ ). The reference voltage for the ADC is set internally to a 2.56V in the program.

### Program Flow

- Including necessary library files
- Initializing the variables
- Initializing object for I2C
- Waiting for master request
- If master requests, read 3 ADC values
- Send the measured values to the master
- Again waiting for another master request

### Program

```
#include <TinyWire.h>

int16_t ph; int16_t moisture; int16_t light; //variables for saving data

void setup() {

    analogReference(INTERNAL2V56);

    TinyWire.begin(1); // join i2c bus with address #1

    TinyWire.onRequest(requestEvent); // register event

}

void loop() {

    delay(100);

}

void requestEvent() { // function that executes whenever data is requested by master

    // this function is registered as an event, see setup()

    ph = analogRead(A0);

    moisture = analogRead(A3);

    light = analogRead(A2);

    byte myArray1[2];
```

```

byte myArray2[2];

byte myArray3[2];

myArray1[0] = (ph >> 8) & 0xFF;

myArray1[1] = ph & 0xFF;

TinyWire.send(myArray1, 2);

myArray2[0] = (moisture >> 8) & 0xFF;

myArray2[1] = moisture & 0xFF;

TinyWire.send(myArray2, 2);

myArray3[0] = (light >> 8) & 0xFF;

myArray3[1] = light & 0xFF;

TinyWire.send(myArray3, 2);

}

```

## Observations

Data that are received in the PC serial monitor.

```

COM7
ph0; light492; moisture4
ph1; light304; moisture76
ph0; light281; moisture816
ph0; light294; moisture690
ph0; light306; moisture648
ph0; light316; moisture628
ph0; light314; moisture614
ph1; light312; moisture606
ph0; light312; moisture598
ph1; light312; moisture593
ph0; light310; moisture589
ph0; light307; moisture585
ph0; light304; moisture582
ph0; light302; moisture579
ph0; light300; moisture577

[Autoscroll checked] [Show timestamp unchecked] [Newline] [9600 baud] [Clear output]

Serial.print( ph );
a = Wire.read();
b = Wire.read();
light = a;
light = light << 8 | b;
Serial.print( "; light");
Serial.print( light);
a = Wire.read();
b = Wire.read();
moisture = a;

```

## Finished Ptotype



## Achieved Outcomes

- Successfully transmitted data via I2C bus
- Capable of connecting 128 slave devices (transmitters) parallely to the I2C bus
- Enclosed the PCB in a small enclosure

## Future work

### Migration of communication protocol

Here, the communication protocol used is I2C. The problem with the protocol is that , it is works only in a short distance (few meters). For sensor networking in a large area, it is important to use a long distance protocol. So in the future development faces the protocol should be changed .

### Wireless tansmission

The migration from wire communication to wireless communication should reduce the complexity and cost by avoiding the wiring.